

Temperature Sensor

Objective: Using BJT to make a circuit that can indicate the temperature.

In the shown circuit:

By Applying KVL:

$$V_{out} = (V_{CC} - V_{BE1}) - (V_{CC} - V_{BE2})$$

$$V_{out} = V_{BE2} - V_{BE1}$$

From the BJT char. Eq. ($I_C = I_S e^{\frac{V_{BE}}{V_t}}$)

$$V_{BE} = V_t \ln\left(\frac{I_C}{I_S}\right) \text{ So,}$$


$$V_{out} = V_t \ln\left(\frac{I_{C2}}{I_{S2}}\right) - V_t \ln\left(\frac{I_{C1}}{I_{S1}}\right)$$

$$V_{out} = V_t \ln\left(\frac{I_{C2} \times I_{S1}}{I_{S2} \times I_{C1}}\right), \text{ Assuming the transistors are identical } (I_{S1} = I_{S2})$$

And since $I_{C1} = I_1$, $I_{C2} = I_2$, $V_t = \frac{KT}{q}$

$$V_{out} = \frac{KT}{q} \ln\left(\frac{I_2}{I_1}\right), \quad V_{out} = \frac{K}{q} \ln\left(\frac{I_2}{I_1}\right) \times T$$

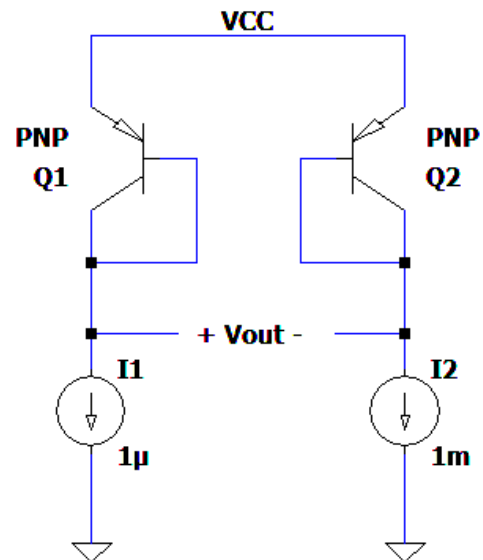So the output of this circuit varies linearly with the temperature



but the value of the term $\frac{K}{q} \ln\left(\frac{I_2}{I_1}\right)$ is small even after using a higher current ratio.

1. The output could be further amplified by using a simple differential amplifier circuit.
2. Or we could adjust the current ratio to get the desired output

✚ Assume we want to represent the temperature as millivolts

$$\text{So } \frac{K}{q} \ln\left(\frac{I_2}{I_1}\right) = \frac{1}{1000}, \left(\frac{K}{q} \cong 8.66 \times 10^{-5}\right)$$

$$\ln\left(\frac{I_2}{I_1}\right) = 11.54, \frac{I_2}{I_1} = 103501.78 \text{ (if } I_1 = 0.1\mu A\text{)}$$

$$\text{Then } I_2 = 10.35\text{mA}$$

$$\text{Then } V_{out} = T \text{ mV (T is in kelvin)}$$